

H bridge basics

Fabien Le Mentec

`texane@gmail.com`

Abstract

This document describes the basics of H bridges. The primary goal is to learn more about electronics.

1 Introduction

1.1 Purpose

I wanted a small project to learn more about electronics basics. Since I regularly need to drive a DC motors, I chose to work on a home made H bridge board described in this document. Note that the circuit uses off the shelf parts and can be more complicated than needed and not efficient. A real application should use packaged H bridge circuits.


2 Features

The board features:

- 3 wires, safe H signaling interface, avoiding invalid transistor states
 - PWM,
 - FORWARD,
 - BRAKE.
- controlling software
 - coding done by XXX
- power stage driving up to XXX motors.


3 H bridge theory of operation

 An H bridge is a circuit allowing to drive DC motors in both direction. The name comes from the typical circuit graphical representation which looks like the 'H' alphabet letter.




H bridge circuit

 
QXX are transistors allowing the current flowing through the DC motor to be electrically controlled. I am interested in 3 configurations:



FORWARD mode

 

REVERSE mode

 

BRAKE mode

4 H signaling interface

The H bridge expects a correct transistor configuration to work. Even worth, an incorrect setup can damage the circuit and motor. I designed a 3 wire signaling interface, called the H signaling interface, to address this issue:

<i>Name</i>	<i>Description</i>
FWD	controls the motor direction
PWM	controls the motor speed
BRAKE	slow the motor down until it stops

H control signals

Since I have a software background it is easier for me to think in terms of C programming control structures. I thus express the H state machine in a C code which I then translate into logical statements. I use the resulting statement set to design the H state circuit using electronic gates.

```
if (BRAKE == 0)
{
    if (FWD == 1)
    {
        Q01 = 0;
        Q10 = 0;
        Q11 = 1;


        Q00 = PWM;
    }
    else /* REVERSE */
    {
        Q00 = 0;
        Q01 = 1;
        Q11 = 0;

        Q10 = PWM;
    }
}
else /* (BRAKE == 1) */
{
    Q00 = 1;
    Q01 = 1;
    Q10 = 1;
    Q11 = 1;
}
```

The above code reduces to the following set of logical statments:

Q00 = (FWD & PWM)		BRAKE;
Q01 = (!FWD)		BRAKE;
Q10 = ((!FWD) & PWM)		BRAKE;
Q11 = FWD		BRAKE;

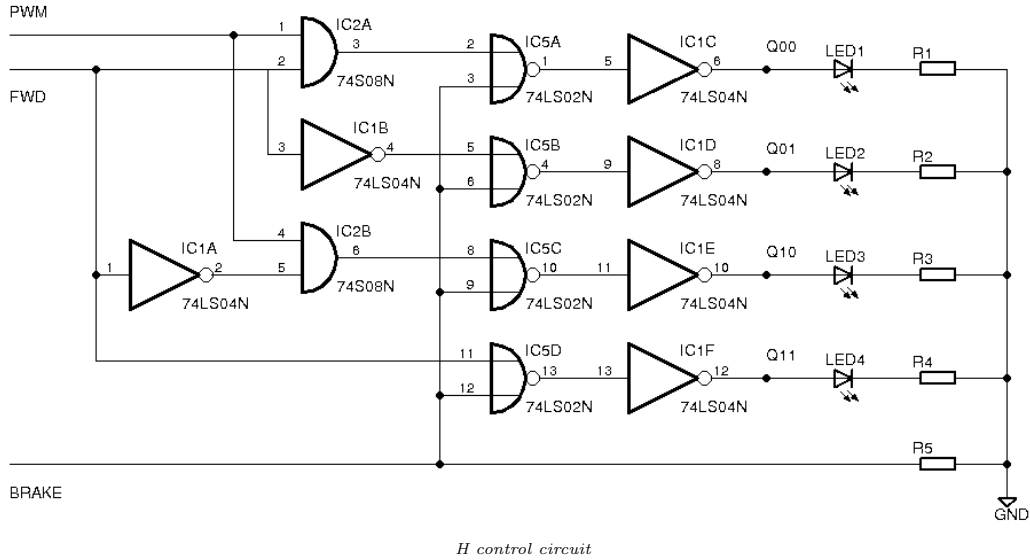These 4 statements are implemented by the following circuit:




Note that I do not have OR gates, so I used NOR gates and inverters. It complexifies the circuit a bit. Apart from that, the logical statements are naively implemented using electronic gates.

<i>Reference</i>	<i>Quantity</i>	<i>Description</i>
SN74LS02N	1	quad 2 input NOR gates
SN74LS04N	1	hex inverter
SN74LS08N	1	quad 2 input AND gates
Resistors	5	2.4k ohms
LEDS	4	

part list

 Picture of the prototyped circuit, with switches added for testing:



H control circuit prototype

5 Power stage

TODO

6 PWM generation

IN PROGRESS

6.1 PWM basics

The motor speed is controlled using a PWM signal.


TODO: explain duty cycle, averaged total current as a function of time

6.2 PWM using transistors


TODO

 6.3 PWM using a NE555

I use a NE555 chip in an astable setup to generate a PWM signal. The Philips 555 application note has been used as a reference for this section. The circuit is shown below:



NE555 astable setup

 

NE555 astable circuit

2 things to note:

- a pot is use to control the duty cycle by varying the voltage divider ratio,
- a diode between pins 6 and 7 has been added to allow a duty of less than 50%.

The documentation gives the following formula:

$$Frequency = \frac{1.49}{((Ra+2*Rb)*C1)}$$

In the above circuit, the following values are used:

- $Ra = 0$ to $10k$,
- $Rb = 1k$,
- $C1 = 47n$.

By substitution, we have:

$$\frac{1.49}{(2*10^3+10*10^4)*47*10^{-9}} \leq frequency \leq \frac{1.49}{2*10^3*47*10^{-9}}$$

Thus:

$$2642 \leq frequency \leq 15851$$

- TODO: old result from a different configuration
- TODO: picture of the oscilloscope screen

The frequencies can be checked using an oscilloscope:

$$2272 \leq frequency \leq 10000$$

6.4 PWM using an AVR microcontroller

TODO

7 H controlling software

TODO

8 Status

- PWM / FORWARD / BRAKE signaling interface: PROTOTYPED
- control software: TODO
- power stage: TODO
- documentation: STARTED

9 Conclusion

TODO

10 Further readings

10.1 H bridge projects

- <http://embedded-lab.com/blog/?p=1159>
- <http://www.mcmanis.com/chuck/robotics/tutorial/h-bridge>
- http://www.modularcircuits.com/h-bridge_secrets1.htm
- http://www.solarbotics.net/library/circuits/driver_4varHbridge.html
- http://www.solarbotics.net/library/circuits/driver_buf_h.html
- <http://www.robotroom.com/HBridge.html>
- <http://www.robotroom.com/BipolarHBridge.html>
- http://www.societyofrobots.com/schematics_h-bridgedes.shtml

10.2 Controlling software

- <http://www.seattlerobotics.org/encoder/200001/simplemotor.htm>

11 TODO

- PWM using ne555
 - oscilloscope pictures
 - wider duty cycle range
 - how to compute the duty range
 - more about the 555
- Atmel AVR or ne555 or RC network + variable resistor to control motor speed
- controlling software