

# H bridge basics

Fabien Le Mentec

`texane@gmail.com`

## **Abstract**

This document describes the basics of H bridges. The primary goal is to learn more about electronics.

# **1 Introduction**

## **1.1 Purpose**

I wanted a small project to learn more about electronics basics. Since I regularly need to drive a DC motors, I chose to work on a home made H bridge board described in this document. Note that the circuit uses off the shelf parts and can be more complicated than needed and not efficient. A real application should use packaged H bridge circuits.


## 2 Features

The board features:

- 3 wires, safe H signaling interface, avoiding invalid transistor states
  - PWM,
  - FORWARD,
  - BRAKE.
- controlling software
  - coding done by XXX
- power stage driving up to XXX motors.

 
### 3 H bridge theory of operation

An H bridge is a circuit allowing to drive DC motors in both direction. The name comes from the typical circuit graphical representation which looks like the 'H' alphabet letter.




*H bridge circuit*

 
QXX are transistors allowing the current flowing through the DC motor to be electrically controlled. I am interested in 3 configurations:



*FORWARD mode*

 

*REVERSE mode*

 

*BRAKE mode*

## 4 H signaling interface

The H bridge expects a correct transistor configuration to work. Even worth, an incorrect setup can damage the circuit and motor. I designed a 3 wire signaling interface, called the H signaling interface, to address this issue:

<i>Name</i>	<i>Description</i>
FWD	controls the motor direction
PWM	controls the motor speed
BRAKE	slow the motor down until it stops

*H control signals*

Since I have a software background it is easier for me to think in terms of C programming control structures. I thus express the H state machine in a C code which I then translate into logical statements. I use the resulting statement set to design the H state circuit using electronic gates.

---

```
if (BRAKE == 0)
{
    if (FWD == 1)
    {
        Q01 = 0;
        Q10 = 0;
        Q11 = 1;

        Q00 = PWM;
    }
    else /* REVERSE */
    {
        Q00 = 0;
        Q01 = 1;
        Q11 = 0;

        Q10 = PWM;
    }
}
else /* (BRAKE == 1) */
{
    Q00 = 1;
    Q01 = 1;
    Q10 = 1;
    Q11 = 1;
}
```

---


The above code reduces to the following set of logical statments:

---

Q00 = (FWD & PWM)		BRAKE;
Q01 = (!FWD)		BRAKE;
Q10 = ((!FWD) & PWM)		BRAKE;
Q11 = FWD		BRAKE;

---

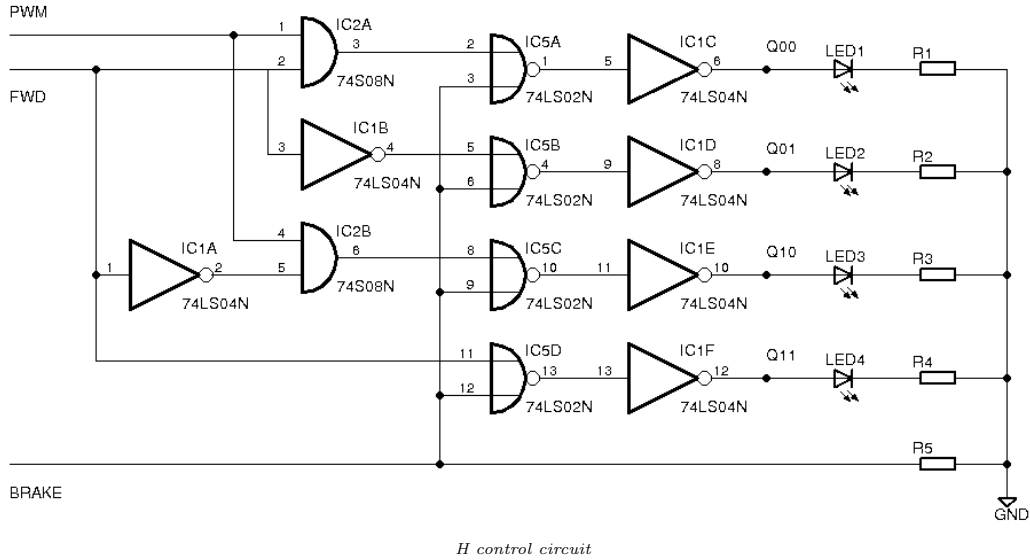These 4 statements are implemented by the following circuit:




Note that I do not have OR gates, so I used NOR gates and inverters. It complexifies the circuit a bit. Apart from that, the logical statements are naively implemented using electronic gates.

<i>Reference</i>	<i>Quantity</i>	<i>Description</i>
SN74LS02N	1	quad 2 input NOR gates
SN74LS04N	1	hex inverter
SN74LS08N	1	quad 2 input AND gates
Resistors	5	2.4k ohms
LEDS	4	


*part list*

 Picture of the prototyped circuit, with switches added for testing:



*H control circuit prototype*

## 5 Power stage

 

*H bridge transistors*

<i>Reference</i>	<i>Quantity</i>	<i>Description</i>
TIP120	2	complementary power darlington transistors
TIP125	2	complementary power darlington transistors
Resistors	4	1.0k

*part list*



## 6 PWM generation

IN PROGRESS

### 6.1 PWM basics

The motor speed is controlled using a PWM signal.


TODO: explain duty cycle, averaged total current as a function of time

### 6.2 PWM using transistors


TODO
 
### 6.3 PWM using a NE555

I use a NE555 chip in an astable setup to generate a PWM signal. The Philips 555 application note has been used as a reference for this section. The circuit is shown below:



*NE555 astable setup*

 

NE555 astable circuit

2 things to note:

- a pot is use to control the duty cycle by varying the voltage divider ratio,
- a diode between pins 6 and 7 has been added to allow a duty of less than 50%.

The documentation gives the following formula:

$$Frequency = \frac{1.49}{((Ra+2*Rb)*C1)}$$

In the above circuit, the following values are used:

- $Ra = 0$  to  $10k$ ,
- $Rb = 1k$ ,
- $C1 = 47n$ .

By substitution, we have:

$$\frac{1.49}{(2*10^3+10*10^4)*47*10^{-9}} \leq frequency \leq \frac{1.49}{2*10^3*47*10^{-9}}$$

Thus:

$$2642 \leq frequency \leq 15851$$

- TODO: old result from a different configuration
- TODO: picture of the oscilloscope screen

The frequencies can be checked using an oscilloscope:

$$2272 \leq frequency \leq 10000$$

## **6.4 PWM using an AVR microcontroller**

TODO

## 7 H controlling software

TODO

## 8 Status

- PWM / FORWARD / BRAKE signaling interface: PROTOTYPED
- control software: TODO
- power stage: TODO
- documentation: STARTED

## 9 Conclusion

TODO

## 10 Further readings

### 10.1 H bridge projects

- <http://embedded-lab.com/blog/?p=1159>
- <http://www.mcmanis.com/chuck/robotics/tutorial/h-bridge>
- [http://www.modularcircuits.com/h-bridge\\_secrets1.htm](http://www.modularcircuits.com/h-bridge_secrets1.htm)
- [http://www.solarbotics.net/library/circuits/driver\\_4varHbridge.html](http://www.solarbotics.net/library/circuits/driver_4varHbridge.html)
- [http://www.solarbotics.net/library/circuits/driver\\_buf\\_h.html](http://www.solarbotics.net/library/circuits/driver_buf_h.html)
- <http://www.robotroom.com/HBridge.html>
- <http://www.robotroom.com/BipolarHBridge.html>
- [http://www.societyofrobots.com/schematics\\_h-bridgedes.shtml](http://www.societyofrobots.com/schematics_h-bridgedes.shtml)

### 10.2 Controlling software

- <http://www.seattlerobotics.org/encoder/200001/simplemotor.htm>

## 11 TODO

- PWM using ne555
  - oscilloscope pictures
  - wider duty cycle range
  - how to compute the duty range
  - more about the 555
- Atmel AVR or ne555 or RC network + variable resistor to control motor speed
- controlling software