An educationnal H bridge board

Fabien Le Mentec texane@gmail.com

Abstract

This document describes an educationnal H bridge board whose prime goal is to learn more about electronics.

1 Introduction

1.1 Purpose

I wanted a small project to learn more about electronics basics. Since I regularly need to drive a DC motors, I chose to work on a home made H bridge board described in this document. Note that the circuit uses off the shelf parts and can be more complicated than needed and not efficient. A real application should use packaged H bridge circuits.


2 Features

The board features:


- 3 wires, safe H signaling interface, avoiding invalid transistor states
 - PWM,
 - FORWARD,
 - BRAKE.
- controlling software
 - coding done by XXX
- power stage driving up to XXX motors.

3 H bridge theory of operation

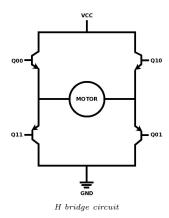An H bridge is a circuit allowing to drive DC motors in both direction. The name comes from the typical circuit graphical representation which looks like the 'H' alphabet letter.



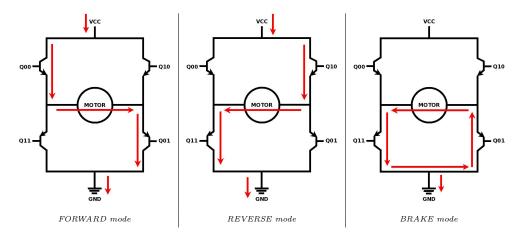QXX are transistors allowing the current flowing through the DC motor to be electrically controlled. I am interested in 3 configurations:



4 H signaling interface

The H bridge expects a correct transistor configuration to work. Even worth, an incorrect setup can damage the circuit. I designed a 3 wire signaling interface to address this issue:

Name	Description	
FWD	controls the motor direction	
PWM	controls the motor speed	
BRAKE	slow the motor down until it stops	

H control signals

Since I have a software background it is easier for me to think in terms of C programming control structures. I thus express the H state machine in a C code which I then translate into logical statements. I use the resulting statement set to design the H state circuit using electronic gates.


```
if (BRAKE == 0)
{
   if (FWD == 1)
   {
     Q01 = 0;
     Q10 = 0;
     Q11 = 1;

     Q00 = PWM;
   }
   else /* REVERSE */
   {
     Q00 = 0;
     Q01 = 1;
     Q11 = 0;

     Q10 = PWM;
   }
}
else /* (BRAKE == 1) */
{
     Q00 = 1;
     Q01 = 1;
     Q10 = 1;
     Q01 = 1;
     Q10 = 1;
     Q10 = 1;
     Q11 = 1;
     Q11 = 1;
}
```

The above code reduces to the following set of logical statuents:

```
Q00 = (FWD & PWM) | BRAKE;
Q01 = (!FWD) | BRAKE;
Q10 = ((!FWD) & PWM) | BRAKE;
Q11 = FWD | BRAKE;
```

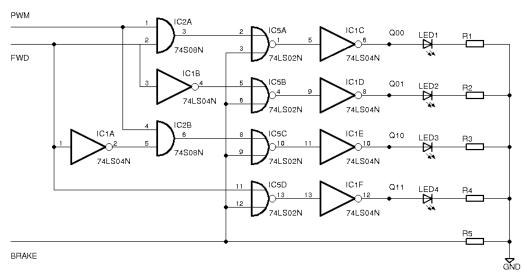

These 4 statements are implemented by the following circuit:


 $H\ control\ circuit$

Note that I do not have OR gates, so I used NOR gates and inverters. It complexifies the circuit a bit. Apart from that, the logical statements are naively implemented using electronic gates.

Reference	Quantity	Description
SN74LS02N	1	quad 2 input NOR gates
SN74LS04N	1	hex inverter
SN74LS08N	1	quad 2 input AND gates
Resistors	5	2.4k ohms
LEDS	4	

 $part\ list$

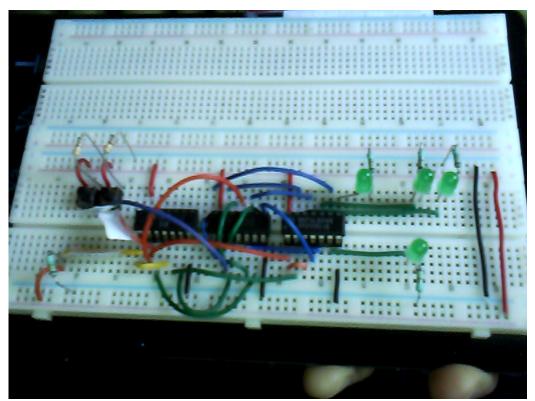Picture of the prototyped circuit, with switchs added for testing:



 $H\ control\ circuit\ prototype$

5 Power stage

6 Controlling software

7 Status

 \bullet PWM / FORWARD / BRAKE signaling interface: PROTOTYPED

ullet control software: TODO

• power stage: TODO

• documentation: STARTED

8 Conclusion

9 Further readings

9.1 H bridge projects

- http://embedded-lab.com/blog/?p=1159
- http://www.mcmanis.com/chuck/robotics/tutorial/h-bridge
- http://www.modularcircuits.com/h-bridge_secrets1.htm
- http://www.solarbotics.net/library/circuits/driver_4varHbridge.html
- $\bullet \ http://www.solarbotics.net/library/circuits/driver_buf_h.html$
- http://www.robotroom.com/HBridge.html
- http://www.robotroom.com/BipolarHBridge.html

9.2 Controlling software

• http://www.seattlerobotics.org/encoder/200001/simplemotor.htm

- ne555 + variable resistor to control motor speed
- controlling software